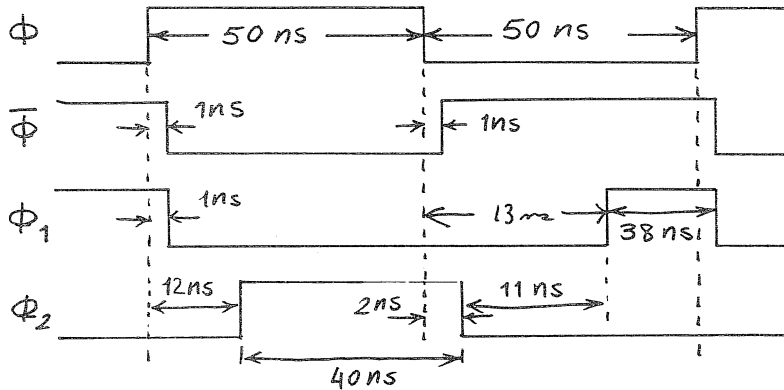


## Chapter 10 - Problems

- 10.1) The clock period is  $\frac{1}{10 \text{ MHz}} = 100 \text{ ns}$ . Assuming 50 % duty cycle, we have the following timing diagram:



(not to scale)

10.2)  $C_2 V_o(n) = C_2 V_o(n-1) - C_1 V_i(n)$

$$\Rightarrow C_2 V_o(z) = C_2 z^{-1} V_o(z) - C_1 V_i(z) \Rightarrow \frac{V_o(z)}{V_i(z)} = \frac{-C_1/C_2}{1 - z^{-1}}$$


- 10.3)  $C_{P2}$  is always discharged since its voltage is virtually ground.

During  $\Phi_1$ ,  $C_{P1}$  is charged to  $V_i(n) C_{P1}$ .

This charge will be transferred

to  $C_2$  during  $\Phi_2$ . Therefore:  $C_2 V_o(n) = C_2 V_o(n-1) - C_{P1} V_i(n-1) - C_1$
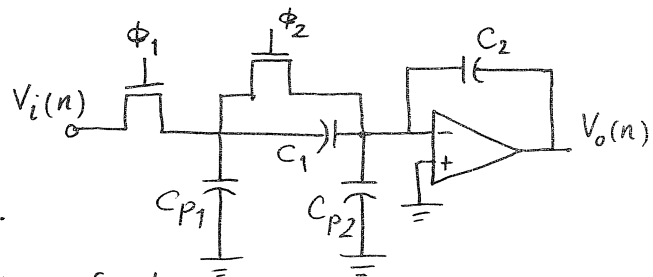
$$\Rightarrow \frac{V_o(z)}{V_i(z)} = - \frac{\frac{C_1}{C_2} + \frac{C_{P1}}{C_2} z^{-1}}{1 - z^{-1}}$$



10.4) A finite gain of  $A$  implies the voltage of the inverting terminal is  $-\frac{1}{A} V_o(n)$  if the output voltage is  $V_o(n)$ .

$$C_2 V_o(n) \left[1 + \frac{1}{A}\right] = C_2 V_o(n-1) \left[1 + \frac{1}{A}\right] - C_1 \left[V_i(n-1) + \frac{V_o(n)}{A}\right]$$

Note that at the end of  $\Phi_2$ , the voltage across  $C_1$ , which is  $V_i(n-1)$ , reduces to  $-\frac{V_o(n)}{A}$ , not ground.

Also, assuming  $\frac{1}{A} \ll 1$ , we have

$$C_2 V_o(n) = C_2 V_o(n-1) - C_1 \left(V_i(n-1) + \frac{V_o(n)}{A}\right)$$

$$\Rightarrow \frac{V_o(z)}{V_i(z)} = \frac{-C_1/C_2}{z(1 + \frac{C_1}{C_2 A}) - 1}$$

At dc ( $z=1$ ), this gain is equal to  $\frac{-C_1/C_2}{1 + \frac{C_1}{C_2 A} - 1} = -A$

$$Z_P = \frac{1}{1 + \frac{C_1}{C_2 A}} = 1 - \frac{C_1}{C_2 A} \quad \text{assuming } C_1 \ll C_2 A.$$

$$10.5) \quad H(z) = \frac{Kz}{z - 0.53327}$$

$$\text{Setting } H(1) = 1 \Rightarrow H(z) = \frac{0.46673z}{z - 0.53327}$$

Equating  $H(z)$  with that of Eq. (10.33) and assuming

$$C_A = 10 \text{ pF} \Rightarrow \underbrace{C_1 = 0} \quad \underbrace{C_2 = -8.752 \text{ pF}} \quad , \quad \underbrace{C_3 = 8.752 \text{ pF}}$$

$$\text{The new gain at } 50 \text{ kHz} = \underline{\underline{H(-1) = -0.304 = -10.3 \text{ dB}}}$$

$$10.6) \quad \omega_{3dB} = \frac{1 \text{ kHz}}{50 \text{ kHz}} \times 2\pi = 0.04\pi \text{ RAD/SAMPLE}$$

Since the zero is at 0 rather than -1, we cannot use a bilinear transform. From example 9.5 in chapter 9, we have

$$\omega_{3dB} = \cos^{-1} \left( 2 - \frac{a}{2} - \frac{1}{2a} \right)$$

This example assumed a zero at  $\infty$  which has same magnitude response as a zero at 0.

$$\cos(0.4\pi) = 2 - \frac{a}{2} - \frac{1}{2a} \Rightarrow a = 0.8821$$

$$H(z) = \frac{kz}{z - 0.8821} \quad \text{Forcing } H(1) = 1 \Rightarrow k = 0.1179$$

Equating coeff with (10.33) results in

$$\underline{C_1 = 0}, \quad \underline{-C_2 = C_3 = 6.683 \text{ pF}}$$

$$25 \text{ kHz corresponds to } z = -1, \quad H(-1) = 0.0626 = \underline{-24.1 \text{ dB}}$$

10.7) The transfer function is given by (10.33). Substituting the given capacitances, we have:


$$\underline{H(z) = \frac{0.1z}{1.1z - 1}}$$

$$\text{At dc: } z=1, \quad \underline{H(1) = 1}, \quad \cancel{H(1) = 0}$$

$$\text{At } f_{s/4}: z=j, \quad \underline{H(j) = 0.673 \angle -42.27^\circ}$$

$$\text{At } f_{s/2}: z=-1, \quad \underline{H(-1) = 0.0476 \angle 0^\circ}$$

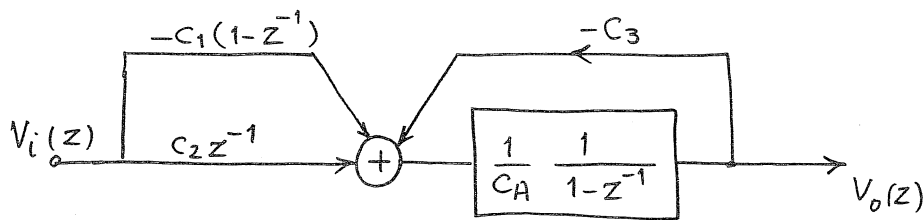10.8) The equivalent signal flow graph is:



$$\left\{ V_i(z) [C_2 z^{-1} - C_1 + C_1 z^{-1}] - C_3 V_o(z) \right\} \frac{1}{C_A} \frac{1}{1-z^{-1}} = V_o(z)$$

$$\Rightarrow H(z) = \frac{V_o(z)}{V_i(z)} = - \frac{C_1 - (C_1 + C_2) z^{-1}}{(C_A + C_3) - C_A z^{-1}}$$


---

10.9) The transfer function poles are the zeros of the denominator.

Using (10.49) with  $K_6 = 0$ , we have

$$z^2 + (K_4 K_5 - 2)z + 1 = 0$$

Since all the coefficients are real numbers, this equation has, in general, two complex conjugate roots,  $z_1$  &  $z_1^*$ , with their product equal to the constant term of the equation (i.e. 1).

$$\therefore z_1 z_1^* = 1 \Rightarrow |z_1|^2 = 1 \Rightarrow |z_1| = 1$$

$\therefore$  both  $z_1$  &  $z_1^*$  lie on the unit circle.

$$10.10) \quad \omega_0 = \frac{2\pi}{100} = 0.062832 \text{ RAD/SAMPLE} \quad \& \quad Q = 20$$

$$\text{Equivalent } \Omega_0 = \tan\left(\frac{\omega_0}{2}\right) = 0.0314263 \text{ RAD/S}$$

$$\therefore H_a(s) = \frac{\frac{\omega_0}{Q} s}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2} = \frac{0.0015713 s}{s^2 + 0.0015713 s + 0.00098761}$$

Transform using the bilinear transform  

$$s = \frac{z-1}{z+1}$$

$$H(z) = \frac{0.001572 z^2 - 0.001572}{1.003145 z^2 - 1.9991875 z + 1}$$

FOR Low-Q biquad from (10.51) - (10.56)

$$k_3 = -0.001572 \quad k_2 = 0.003144$$

$$k_6 = 0.003145 \quad k_4 = k_5 = 0.06291$$

$$k_1 = 0$$

FOR HIGH-Q biquad from (10.69) - (10.74)

$$H(z) = \frac{0.001567 z^2 - 0.001567}{z^2 - 1.99292 z + 0.99687}$$

$$k_3 = 0.001567 \quad k_1 = 0 \quad k_2 = 0.0499$$


$$k_4 = k_5 = 0.06285 \quad k_6 = 0.0498$$

Ignoring  $k_3$  (since it only sets zero at -1)

CAP ratio for low-Q is 318 while it is 20 for high-Q biquad.

- 14.18** Using the bilinear transform, find the transfer function in the z-domain of a discrete-time bandpass filter with a  $Q = 20$  (in the continuous-time domain) and a peak gain of one near  $f_s/100$ . Find the largest to smallest capacitor ratio if this transfer function is realized using the high-Q biquad circuit, and compare it to that which would be obtained if the low-Q circuit were used instead. Let  $C_1 = C_2 = 1$  in both cases.

10.11)

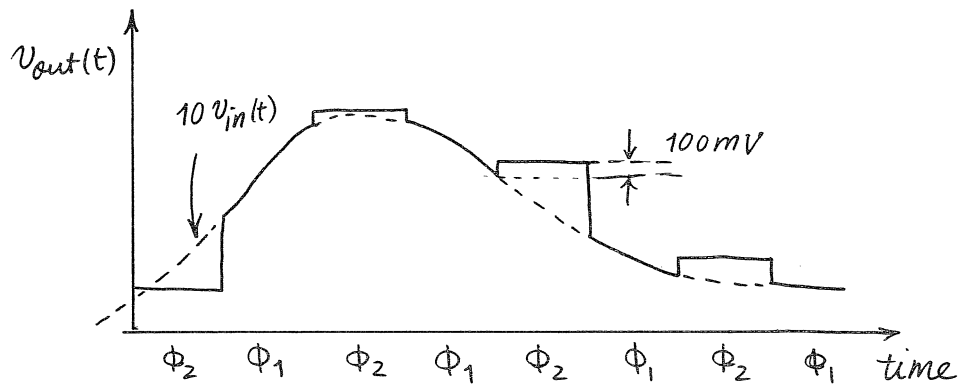

10.12) Assuming  $V_{out} = -V_{ss}$ ,

$$\Delta V_x = -K_2 V_{ss} = -K_{in} V_{in}$$

the positive jump of  $V_x$  is still  $K_1(V_{ss} + V_{DD})$  as before.

$$\Rightarrow T_{osc} = 2 \frac{K_1 (V_{ss} + V_{DD})}{K_2 V_{ss} + K_{in} V_{in}} T$$

Or, equivalently (assuming  $V_{ss} = V_{DD}$ )

$$f_{osc} = \frac{1}{4} \left( \frac{K_2}{K_1} + \frac{K_{in} V_{in}}{K_1 V_{DD}} \right) f$$